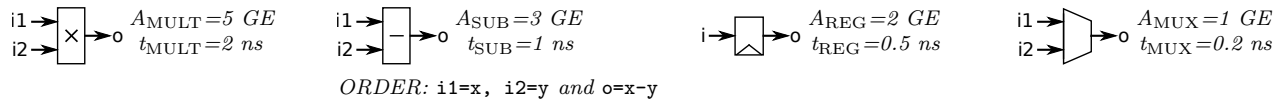


# Essentials of Computer Systems - Exercises #2

## 1 Datapath Design - part 1

### Exercise 1.1 Datapath design:

- (a) Design a datapath (draw a DFD) with the following functionality:  $z = 3(b - a) - ac + a$ . The building blocks available are a multiplier and a subtracter, shown in figure below. You are given an area constraint: you are allowed to use at most 1 multiplier and at most one subtracter.



- (b) Fill out the analysis table for the DFD obtained in part (a) ignoring MUXes:

Analysis table	
latency	
throughput	
critical path delay	
clock period	
# inputs	
# outputs	
# registers	
# subtracters	
# multipliers	
total area in GE	

- (c) Fill out the analysis table for the DFD obtained in part (a) including MUXes:

Analysis table	
latency	
throughput	
critical path delay	
clock period	
# inputs	
# outputs	
# registers	
# multiplexers	
# subtracters	
# multipliers	
total area in GE	

**Exercise 1.2** *Datapath design:*

- (a) Design a datapath (draw a DFD) with the following functionality:  $z = a(a + b) - (bc + a)$ . The building blocks available are a multiplier and an adder, shown in figure below. All inputs are available only in the first clock cycle. The top priority is to minimize the area.



- (b) Fill out the analysis table for the DFD obtained in part (a):

Analysis table	
latency	
throughput	
critical path delay	
clock period	
# inputs	
# outputs	
# registers	
# multiplexers	
# adders	
# multipliers	
total area in GE	

- (c) Draw the circuit for the DFD obtained in part (a):